
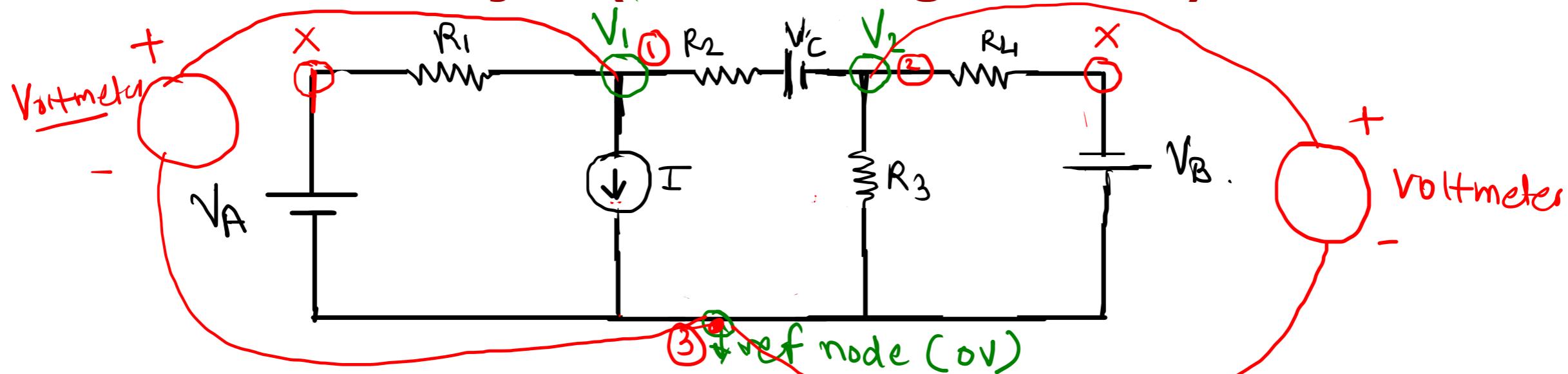


## Nodal Analysis (Node Voltage method)

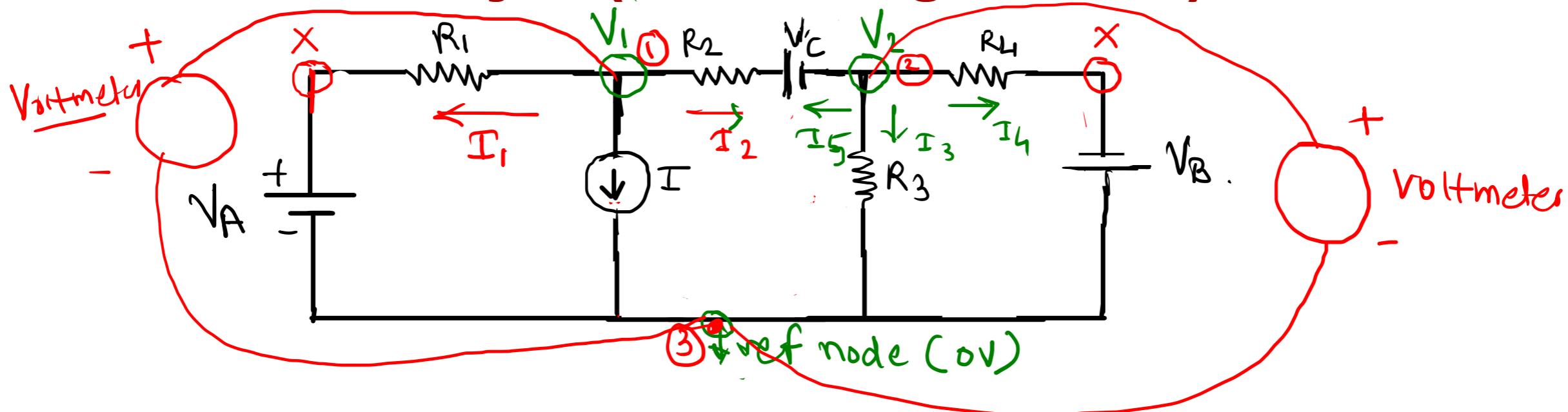

- ⇒ Unknown  $\Rightarrow$  Node Voltage
- ⇒ Identify nodes in given circuit
- ⇒ One node as reference node (Node 3)
- ⇒ Other nodes are called non-reference node (Node 1 & 2)
- ⇒ Non-reference node voltages  $V_1$  &  $V_2$  are assumed to be positive w.r.t. ref. node

## Nodal Analysis (Node Voltage method)



⇒ Apply KCL at non-reference nodes

$$\text{KCL at node } \textcircled{1} \quad I_1 + I_2 + I = 0 \quad \left. \begin{array}{l} \\ \end{array} \right\} \checkmark$$



$$\text{KCL at node } \textcircled{2} \quad I_5 + I_3 + I_4 = 0 \quad \left. \begin{array}{l} \\ \end{array} \right\}$$

⇒ Represents currents in terms of node voltages.

 Using KVL →  $V_1 - I_1 R_1 - V_A = 0$

$$I_1 = \frac{V_1 - V_A}{R_1} \quad \checkmark$$

# Nodal Analysis (Node Voltage method)

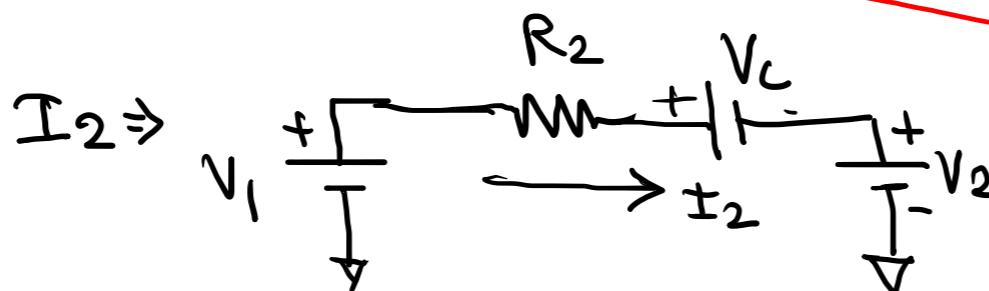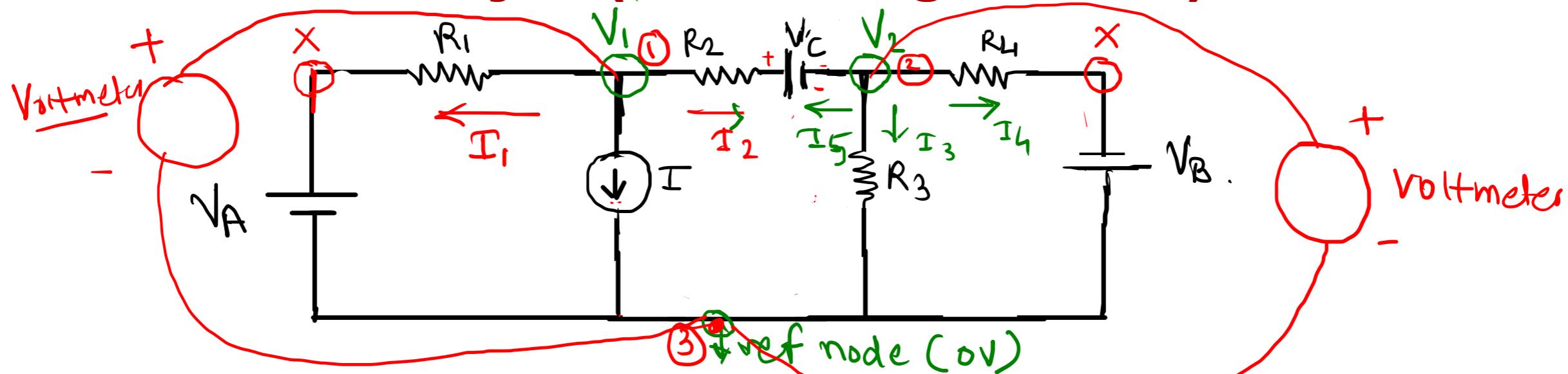

KVL to Loop.

$$V_1 - I_2 R_2 - V_C - V_2 = 0$$

$$I_2 = \frac{V_1 - V_C - V_2}{R_2}$$






KVL to Loop

$$V_2 + V_C - I_5 R_2 - V_1 = 0$$

$$I_5 = \frac{V_2 + V_C - V_1}{R_2}$$

# Nodal Analysis (Node Voltage method)

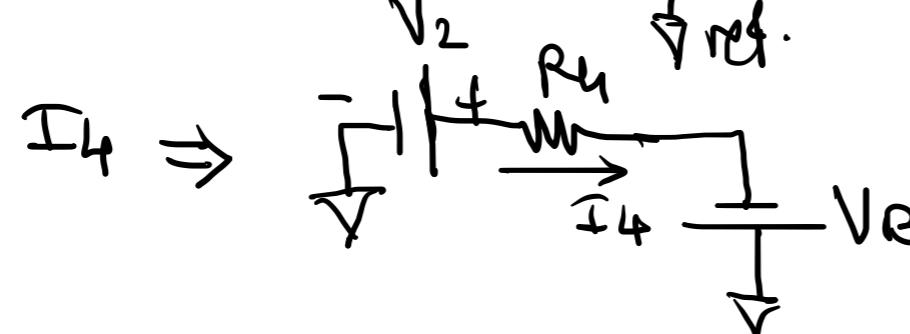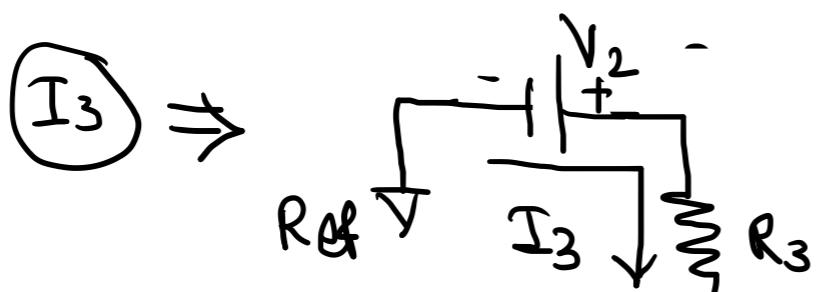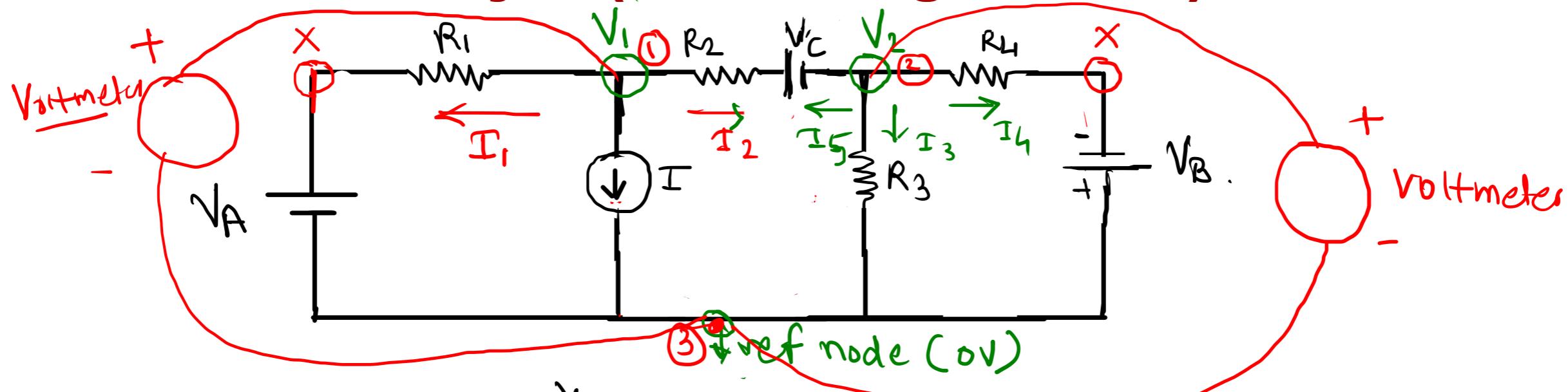

KVL to loop

$$V_2 - I_3 R_3 = 0$$


$$\therefore I_3 = \frac{V_2}{R_3}$$

KVL to loop


$$V_2 - I_4 R_4 + V_B = 0$$

$$I_4 = \frac{V_2 + V_B}{R_4}$$

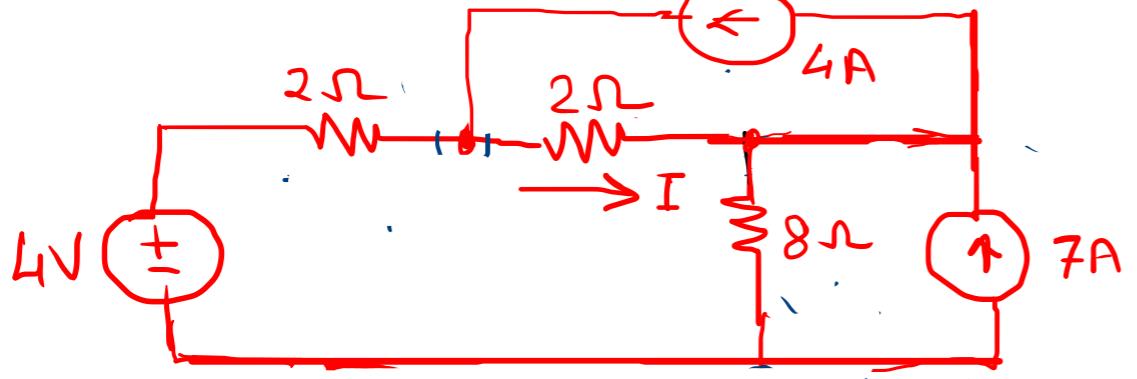① Find Current  $I$  in the following network using Nodal Analysis



$\Rightarrow$

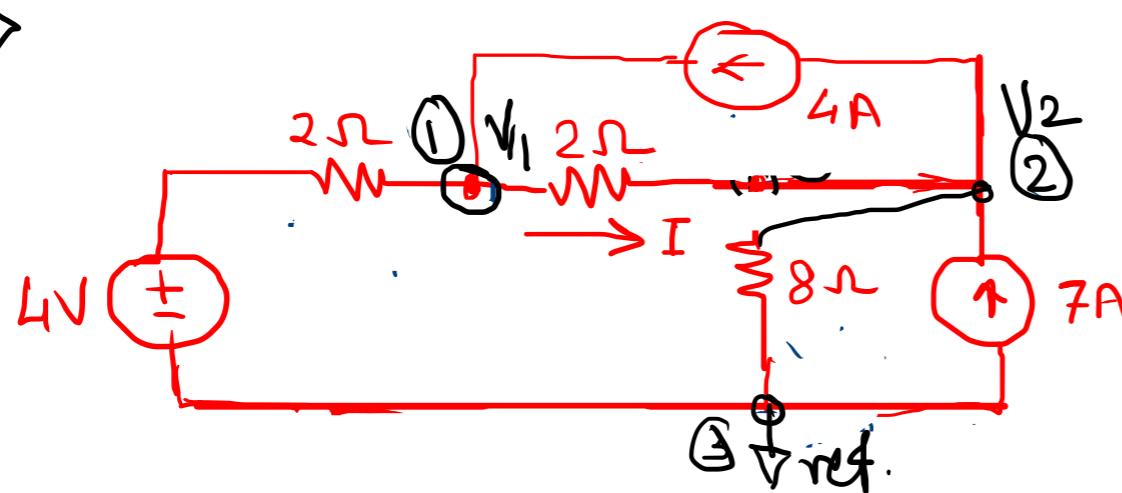

$\Rightarrow$  KCL at node ①

$$\frac{V_1 - 4}{2} + \frac{V_1 - V_2}{2} = 4$$

$$(V_1 - 4) + (V_1 - V_2) = 8$$

$$2V_1 - V_2 = 12 \quad \dots \textcircled{1}$$

KCL at node ②

$$\frac{V_2}{8} + \frac{V_2 - V_1}{2} = 7 - 4$$

$$\frac{V_2 + 4V_2 - 4V_1}{8} = 3$$


$$-4V_1 + 5V_2 = 24 \quad \dots \textcircled{2}$$

Solving ① & ②

$$V_1 = 14V, V_2 = 16V$$

$$I = \frac{V_1 - V_2}{2} = \frac{14 - 16}{2} = \underline{\underline{-1A}} \rightarrow$$

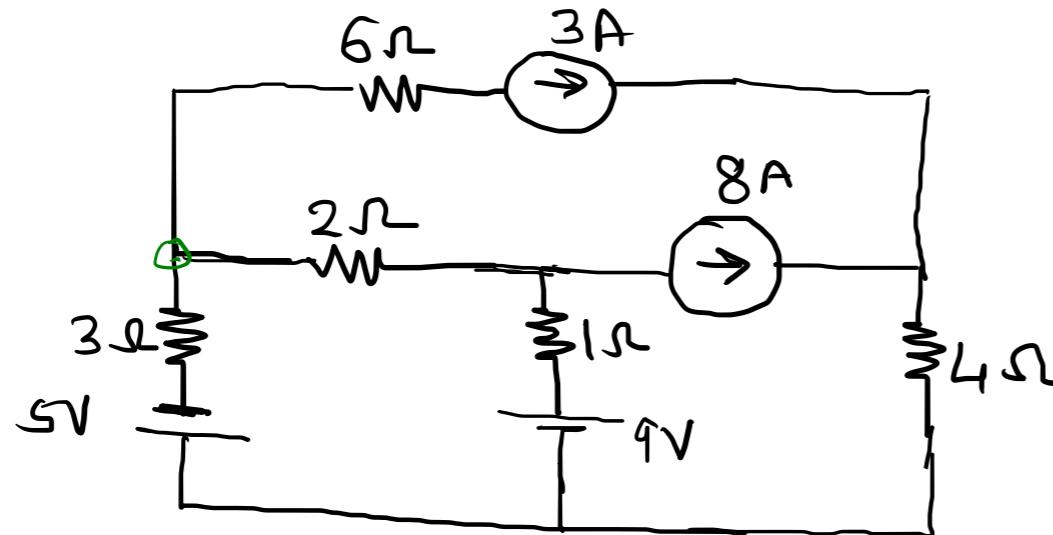Example ② Find Current in  $3\Omega$  Resistor using Nodal Analysis



$\Rightarrow$  KCL at node ①

$$\frac{V_1 + 5}{3} + \frac{V_1 - V_2}{2} + 3 = 0$$

$$\frac{2V_1 + 10 + 3V_1 - 3V_2}{6} = -3$$

$$5V_1 - 3V_2 = -28 \quad \dots \textcircled{1}$$

$\Rightarrow$  KCL at node ②

$$\frac{V_2 - V_1}{2} + \frac{V_2 - 9}{1} + 8 = 0$$

$$V_2 - V_1 + 2V_2 - 18 = -16$$

$$-V_1 + 3V_2 = 2 \quad \dots \textcircled{2}$$

$\Rightarrow$  KCL at

node ③

$$\frac{V_3}{4} = 3 + 8$$

$$V_3 = 11 \times 4 = 44V$$


$$V_1 = -6.5V$$

$$V_2 = -1.5V$$

$$I_3 = \frac{V_1 + 5}{3}$$


$$= \frac{-6.5 + 5}{3} = -0.5A$$

$\Rightarrow$  Identify nodes.

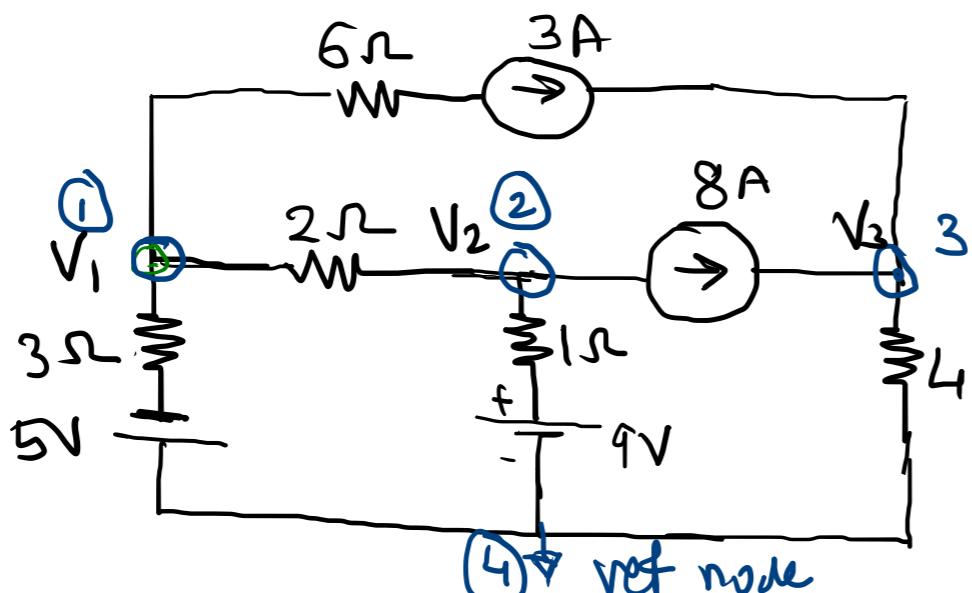

$\Rightarrow$  Type = 2  $\Rightarrow$  Voltage Source without series resistance appearing between Non-reference and reference node.

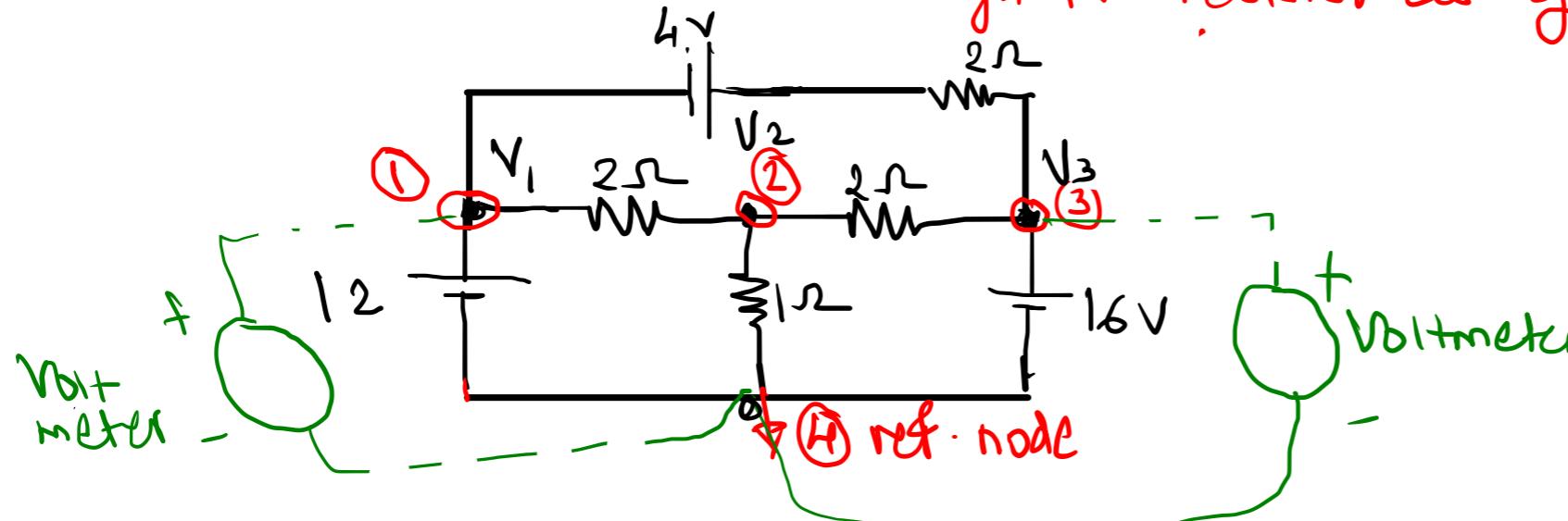$\Rightarrow$  Example ③ Find Current through  $1\Omega$  resistor using Nodal Analysis.



$\Rightarrow$  Identify nodes

$\Rightarrow$  Since 12V & 16V without series resistances appearing between node 1, 3 & ref. node  
so no need to apply KCL.

$$V_1 = 12V \quad \& \quad V_3 = 16V$$

$\Rightarrow$  KCL at node-2

$$\frac{V_2 - V_1}{2} + \frac{V_2 - V_3}{2} + \frac{V_2}{1} = 0$$

$$\frac{V_2 - 12}{2} + \frac{V_2 - 16}{2} + \frac{V_2}{1} = 0$$

$$V_2 - 12 + V_2 - 16 + 2V_2 = 0$$



$$4V_2 = 28$$

$$\boxed{V_2 = 7V}$$

$$I_{1\Omega} = \frac{V_2}{1} = 7A$$


$\Rightarrow$  Type-3 : Voltage Source Without series resistance appearing between two non-reference nodes.

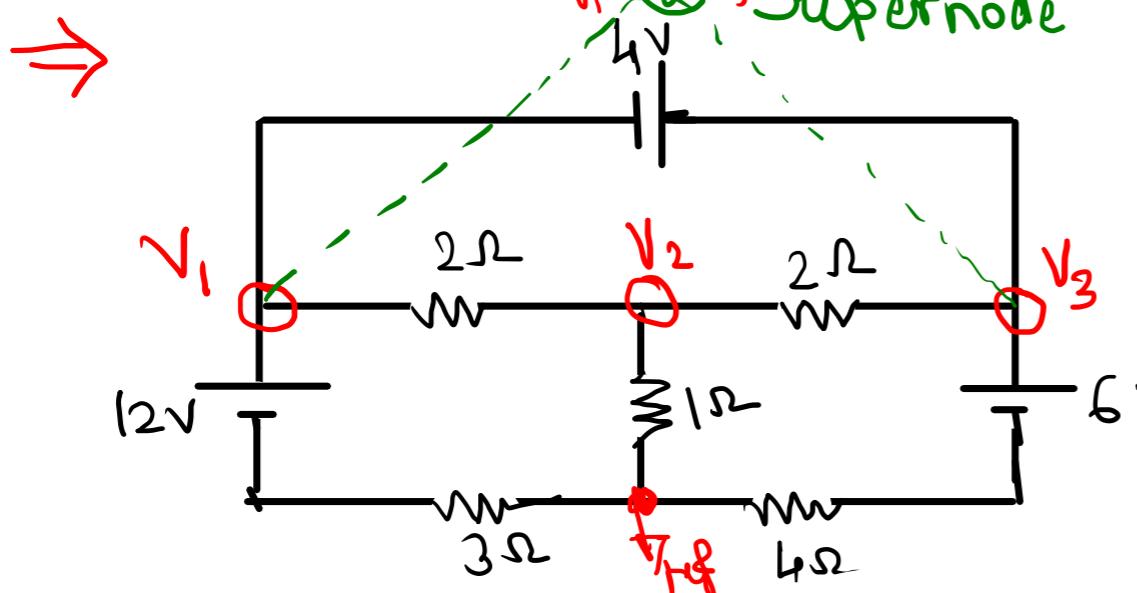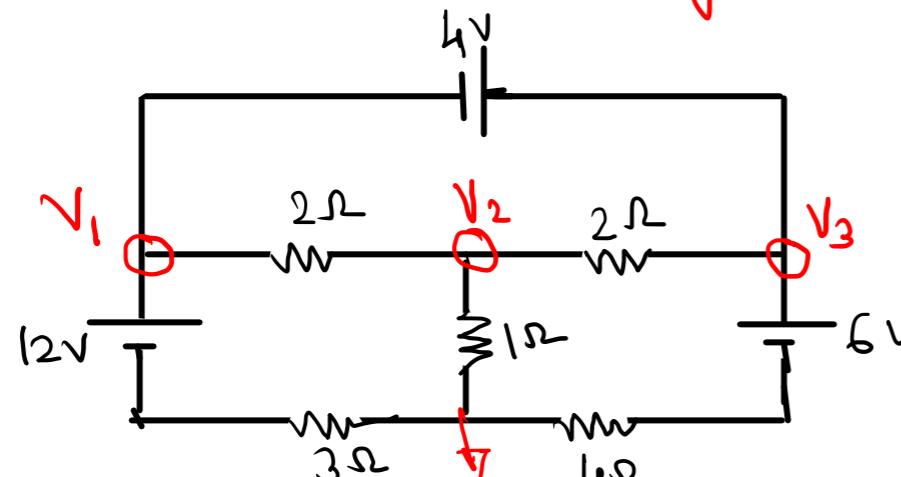Example : find current through  $1\Omega$  resistor



$\Rightarrow$  4V source without series resistance between two non-ref. nodes (1) & (3)

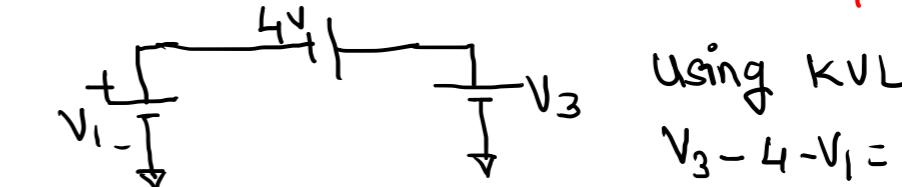$\Rightarrow$  Represent 4V source in terms of  $V_1$  &  $V_3$



$$V_1 - V_3 = -4 \quad \dots \textcircled{1}$$

$\Rightarrow$  Write KCL at supernode keeping  $V_1$  &  $V_3$  intact.

$$\frac{V_1 - V_2}{2} + \frac{V_1 - 12}{3} + \frac{V_3 - V_2}{2} + \frac{V_3 - 6}{4} = 0$$

$$\frac{12}{12} V_1 - 12 V_2 + 4 V_1 - 48 + \frac{2}{2} V_3 - 6 V_2 + 3 V_3 - 18 = 0$$

$$10V_1 - 12V_2 + 9V_3 = 66 \quad \dots \textcircled{2}$$

$\Rightarrow$  KCL to node (2)

$$\frac{V_2 - V_1}{2} + \frac{V_2}{1} + \frac{V_2 - V_3}{2} = 0$$


$$V_2 - V_1 + 2V_2 + V_2 - V_3 = 0$$

$$-V_1 + 4V_2 - V_3 = 0 \quad \dots \textcircled{3}$$


Solving  $\textcircled{1}$ ,  $\textcircled{2}$  &  $\textcircled{3}$   $V_1 = 3.2V$ ,  $V_2 = 2.6V$ ,  $V_3 = 7.2V$

$$I_{1\Omega} = \frac{V_2}{1} = \frac{2.6}{1} = 2.6A$$

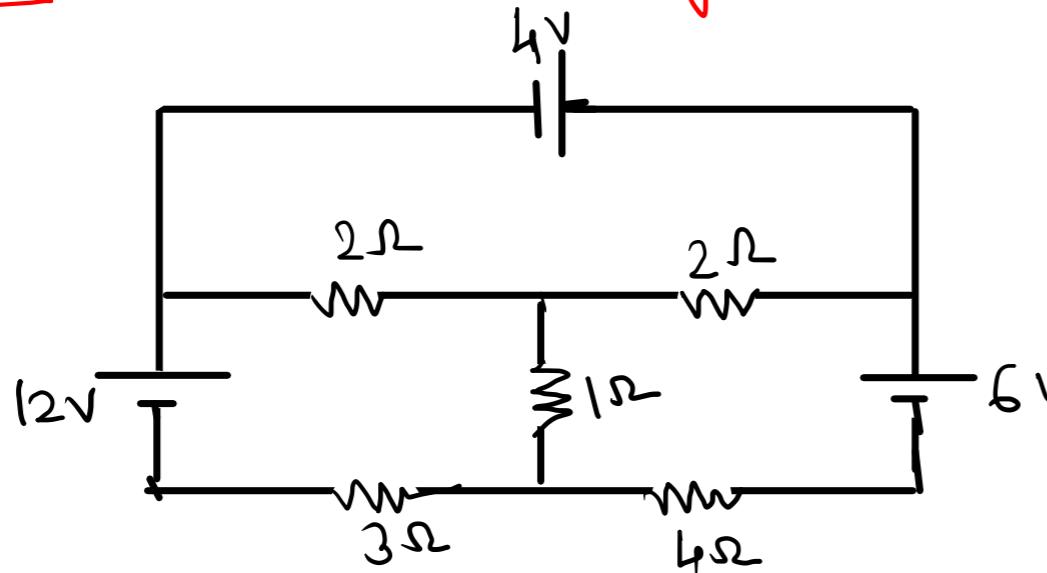Example : find current through  $1\Omega$  resistor



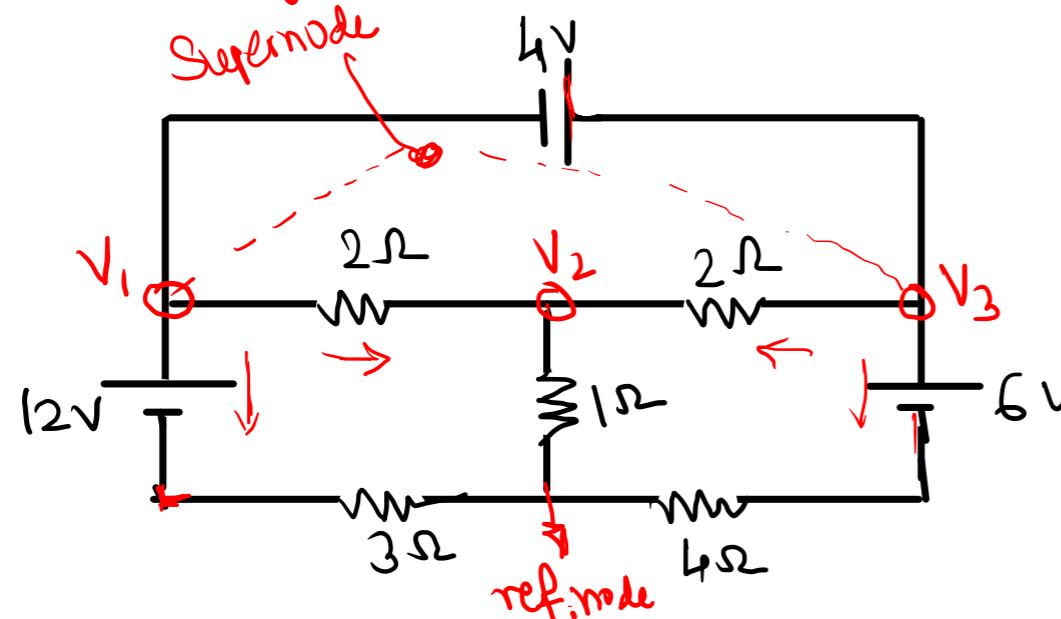$\Rightarrow$  Identify nodes & mark node voltages.



$\Rightarrow$  4V source without series resistance  
between two non-ref nodes (1 & 3)  $\therefore$  it's a case of supernode.

$$\begin{array}{l} \text{+} \\ \text{---} \\ V_1 \\ \text{---} \\ \text{-} \end{array} \quad 4V \quad \begin{array}{l} + \\ \text{---} \\ V_3 \\ \text{---} \\ \text{-} \end{array}$$

$$V_1 + 4 - V_3 = 0$$

$$V_1 - V_3 = -4 \quad \dots \textcircled{1}$$

$\Rightarrow$  KCL to supernode

$$\frac{V_1 - V_2}{2} + \frac{V_1 - 12}{3} + \frac{V_3 - V_2}{2} + \frac{V_3 - 6}{4} = 0$$

$$\frac{V_1 - 6V_2 + 4V_1 - 48 + 6V_3 - 6V_2 + 3V_3 - 18}{12} = 0$$

$$10V_1 - 12V_2 + 9V_3 = 66 \quad \dots \textcircled{2}$$

$\Rightarrow$  KCL to node 2

$$\frac{V_2 - V_1}{2} + \frac{V_2}{1} + \frac{V_2 - V_3}{2} = 0$$

$$\frac{V_2 - V_1 + 2V_2 + V_2 - V_3}{2} = 0$$


$$-V_1 + 4V_2 - V_3 = 0 \quad \dots \textcircled{3}$$

Solving  $\textcircled{1}$ ,  $\textcircled{2}$  &  $\textcircled{3}$

$$V_1 = 3.2V, V_2 = 2.4V, V_3 = 7.2V$$

$$\text{So } I_{1\Omega} = \frac{V_2}{1} = 2.4A$$

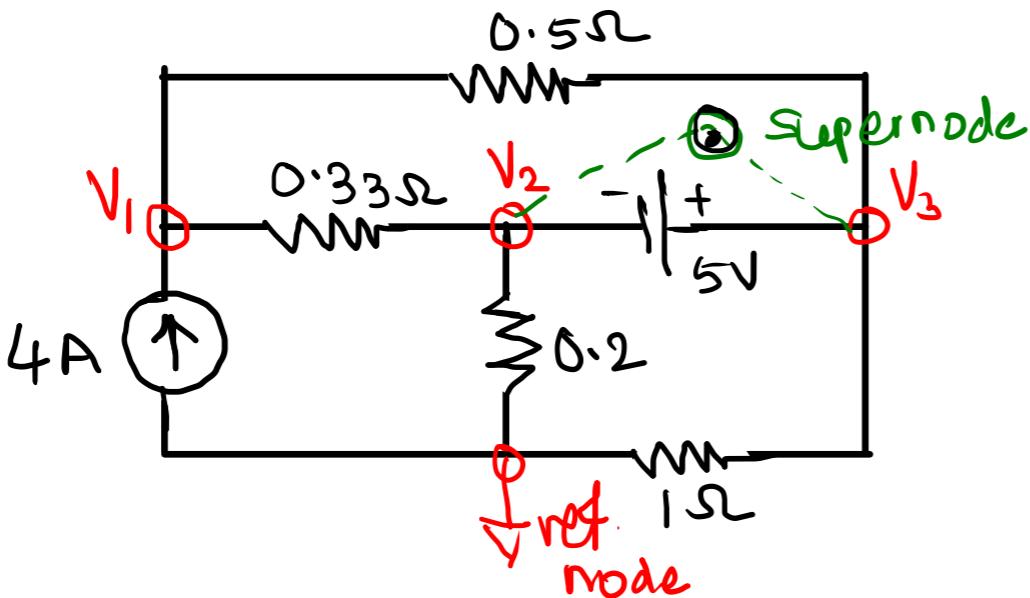Ex. Find  $V_1$ ,  $V_2$  &  $V_3$  in the following circuit using Nodal Analysis.




→ 5V Source without series resistance

between two non-reference nodes

② & ③ so Supernode

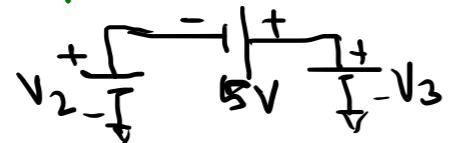→ Represent 5V in terms of  $V_2$  &  $V_3$



$$KVL \quad V_2 + 5 - V_3 = 0$$

$$V_2 - V_3 = -5 \quad \text{--- (1)}$$

⇒ KCL at Supernode

$$\frac{V_2 - V_1}{0.33} + \frac{V_2}{0.2} + \frac{V_3}{1} + \frac{V_3 - V_1}{0.5} = 0$$

$$3.03V_2 - 3.03V_1 + 5V_2 + V_3 + 2V_3 - 2V_1 = 0 \\ -5.03V_1 + 8.03V_2 + 3V_3 = 0 \quad \text{--- (2)}$$

⇒ KCL at node ①


$$\frac{V_1 - V_2}{0.33} + \frac{V_1 - V_3}{0.5} = 4$$

$$3.03V_1 - 3.03V_2 + 2V_1 - 2V_3 = 4$$


$$5.03V_1 - 3.03V_2 - 2V_3 = 4 \quad \text{--- (3)}$$

Solving  $V_1 = 2.63V_2$ ,  $V_2 = -0.16V_3 = 4.83V$   
 ①, ② & ③

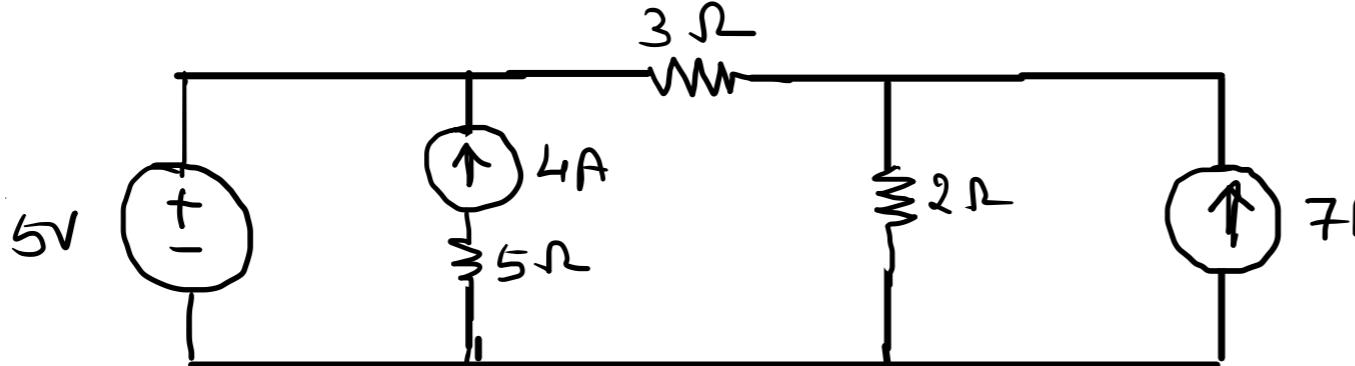Example④ Find voltage across  $2\Omega$  resistor using nodal Analysis



$\Rightarrow$  Solution

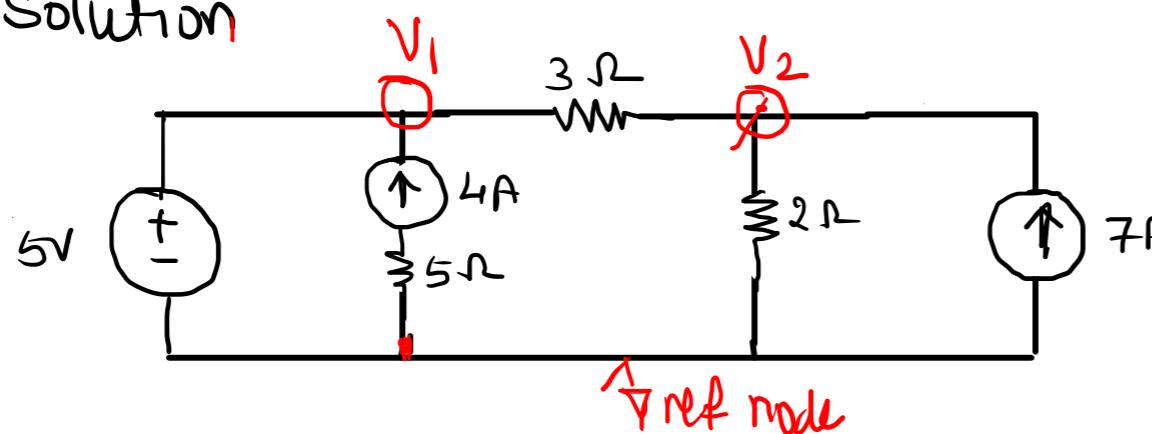

$\Rightarrow$  KCL at node ②

$$\frac{V_2 - V_1}{3} + \frac{V_2}{2} = 7$$

$$\frac{2V_2 - 2V_1 + 3V_2}{6} = 7$$

$$-2V_1 + 5V_2 = 42$$

$$5V_2 = 42 + 2 \times 5$$

$$5V_2 = 52$$


$$V_2 = \frac{52}{5} = 10.4V$$

$$V_{2,e} = \underline{\underline{V_2}} = \underline{\underline{10.4V}}$$


$\Rightarrow$  Voltage SOURCE <sup>without series resistor</sup> appearing between non-ref node ① & ref. node.

$$\text{So } V_1 = 5V.$$

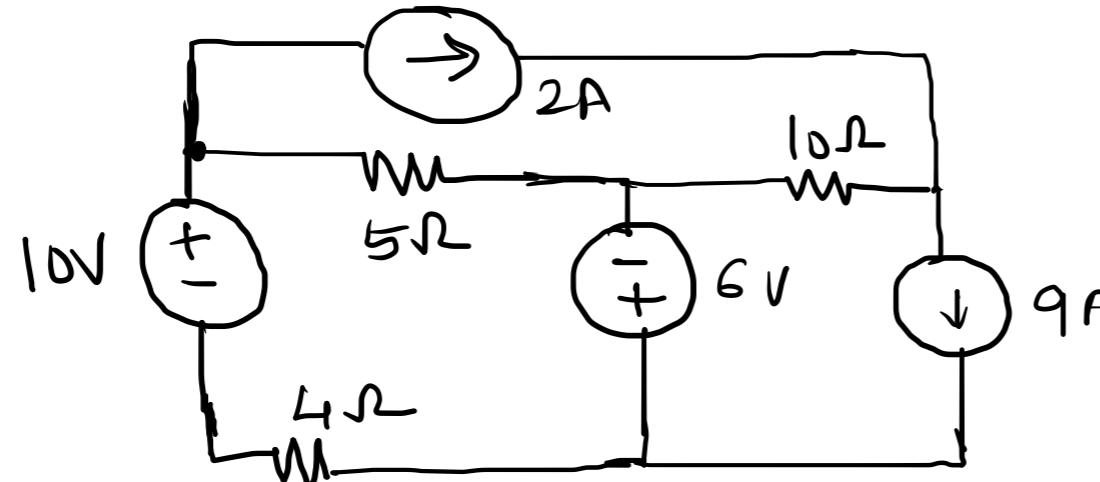Example ⑤ Find power dissipated in  $5\Omega$  resistor using nodal Analysis



⇒ Solution:

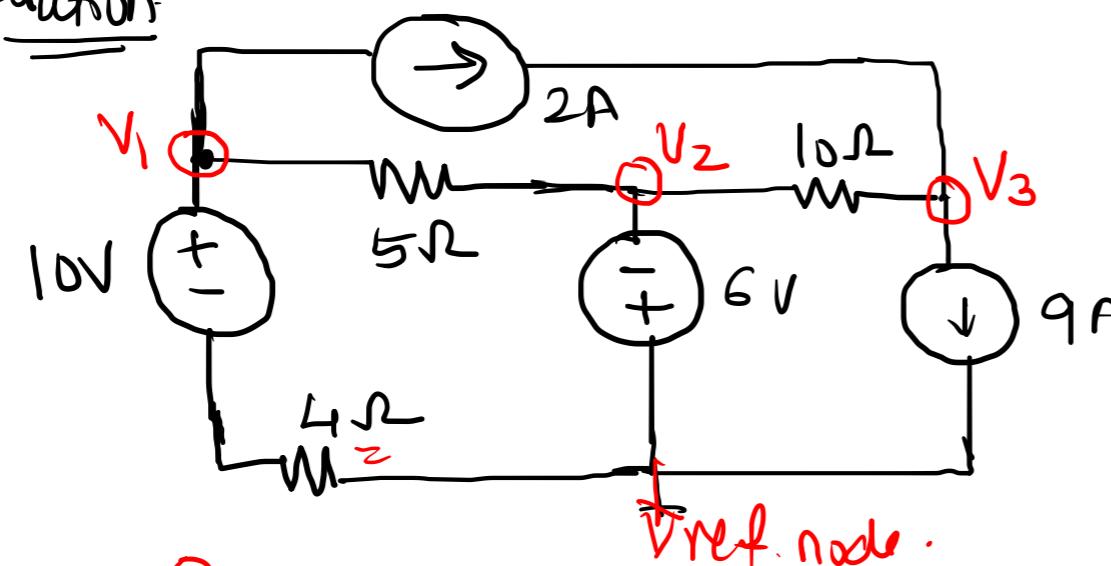

from eqn ①

$$9V_1 - 4V_2 = 10$$

$$9V_1 = 10 + 4V_2 = 10 + 4 \times -6 =$$

⇒ 6V source without series resistance between node ② & ref node

$$\therefore V_2 = -6V$$

⇒ KCL at node ①

$$\frac{V_1 - V_2}{5} + \frac{V_1 - 10}{4} + 2 = 0$$

$$\frac{4V_1 - 4V_2 + 5V_1 - 50 + 40}{20} = 0$$

$$9V_1 - 4V_2 = 10 \quad \dots \dots \textcircled{1}$$

⇒ KCL at node ③


$$\frac{V_3 - V_2}{10} + 9 - 2 = 0$$

$$\frac{V_3 + 6}{10} = -7 \quad | \quad V_3 + 6 = -70$$


$$V_3 = -76V$$

$$\begin{aligned} 9V_1 &= -14 \\ V_1 &= -\frac{14}{9} \end{aligned} \quad | \quad I_{5\Omega} = \frac{V_1 - V_2}{5} = \frac{-14 + 6}{5}$$

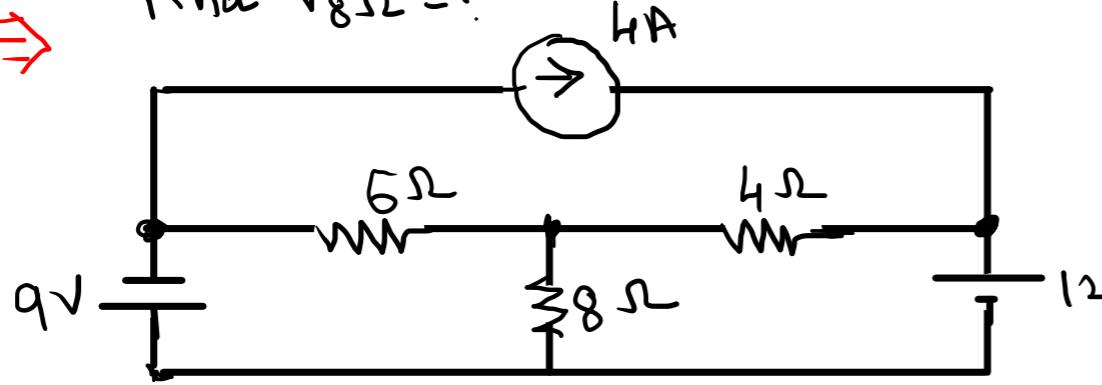Example  $\Rightarrow$  Find  $V_{8\Omega}$  = ?



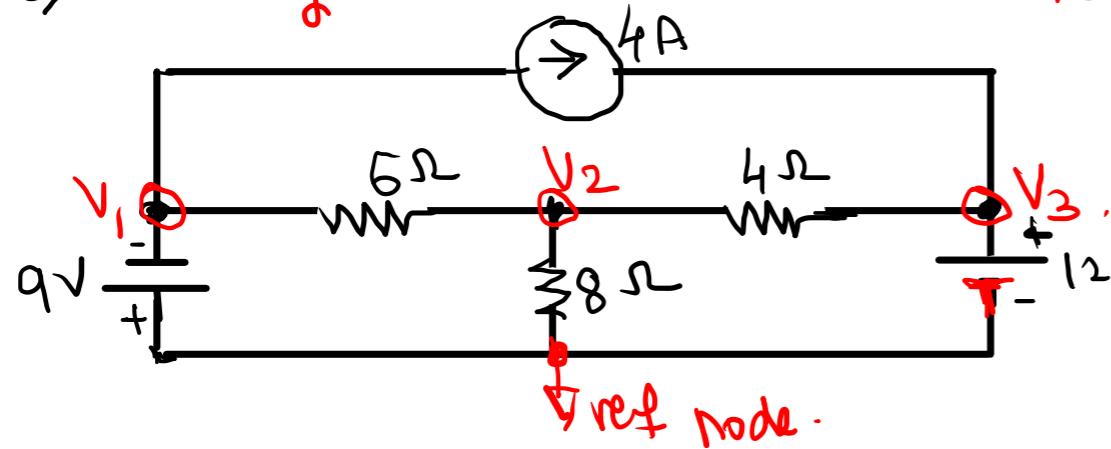$\Rightarrow$  Identify nodes & mark node voltages



$\Rightarrow$  9V without series resistance between node 1 & ref node.

$$\text{So } V_1 = -9V$$

$\Rightarrow$  12V betw node 3 & ref node

$$\text{So } V_3 = 12V$$

$\Rightarrow$  KCL to node 2

$$\frac{V_2 - V_1}{5} + \frac{V_2}{8} + \frac{V_2 - V_3}{4} = 0$$

$$\frac{4V_2 - 4V_1 + 3V_2 + 6V_2 - 6V_3}{24} = 0$$

$$13V_2 - 4V_1 - 6V_3 = 0$$

$$13V_2 = 4 \times -9 + 6 \times 12$$


$$13V_2 = -36 + 72$$

$$13V_2 = 36 \quad V_2 = \frac{36}{13}$$

$$V_{8\Omega} = V_2 = \frac{36}{13}V = 2.76V$$
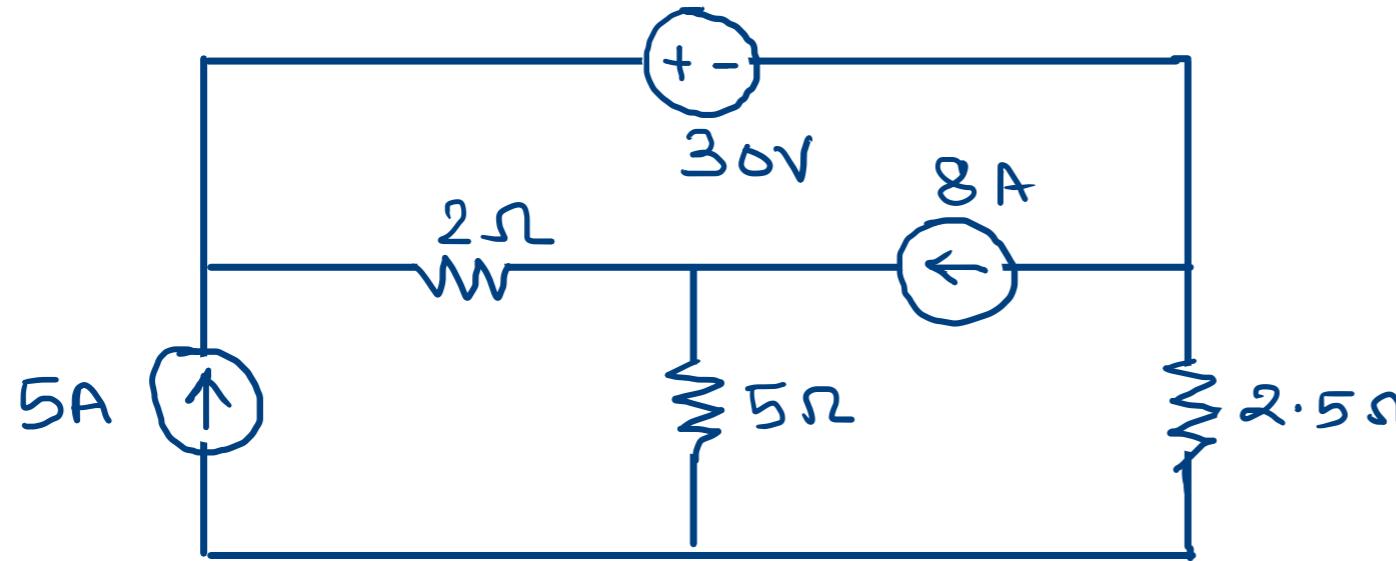
## Practice Numerical

① Find Current in  $2\Omega$  resistor Using Node Analysis.



## Practice Numerical

II Find Current in  $2\Omega$  resistor Using Node Analysis.

